 

CSE 122/222


Non-Volatile Memory

Non-Volatile Memories

The Floating-gate transistor




Device
cross-section

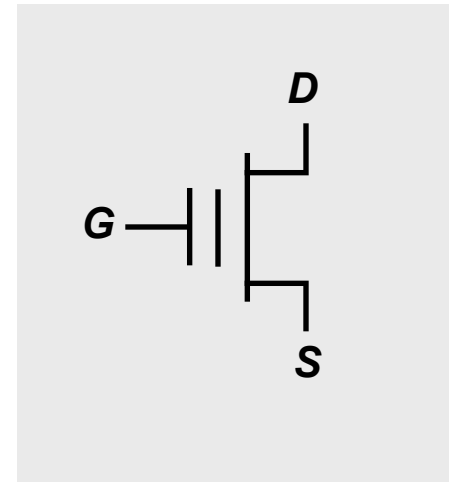


Schematic symbol


Floating-Gate Transistor Programming

 

Avalanche injection

 


 Removing programming voltage leaves charge trapped




Programming results in higher V_T .

A “Programmable-Threshold” Transistor

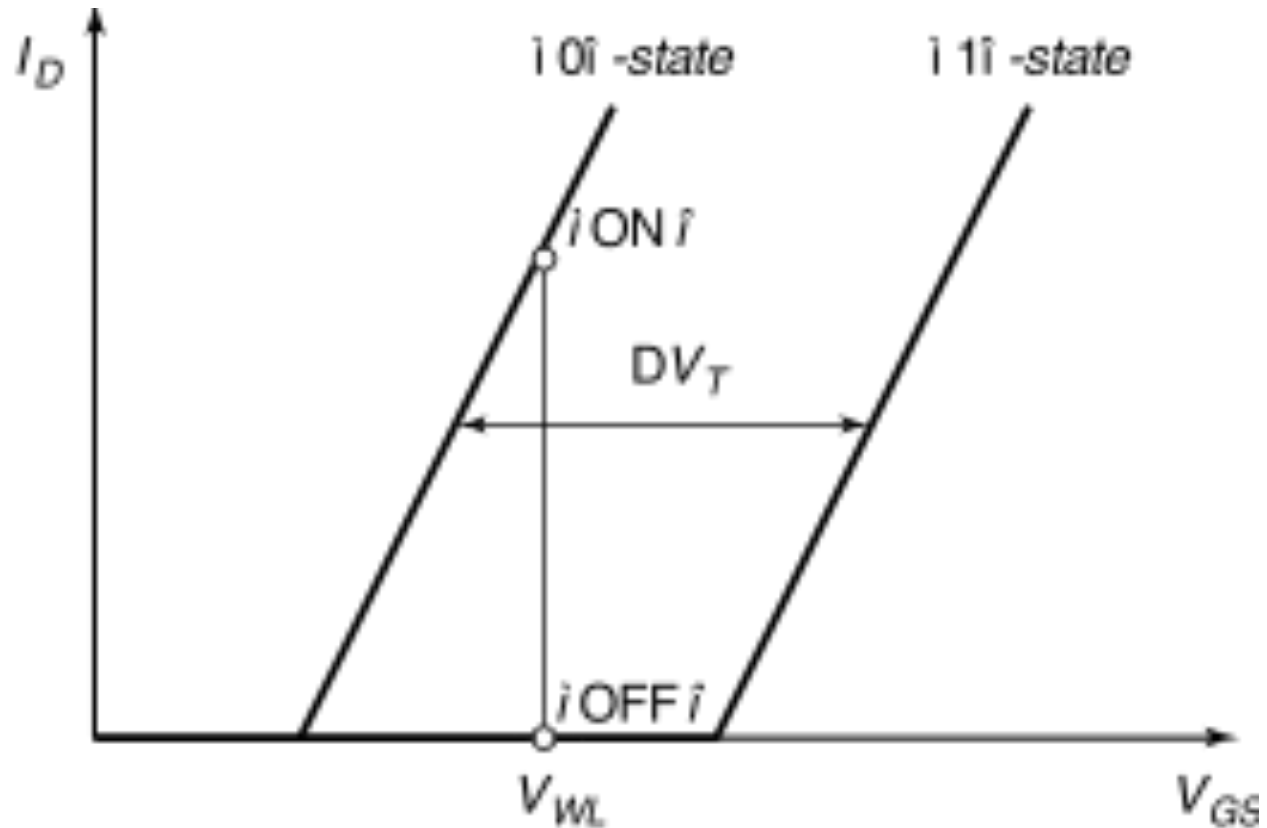


EEPROM Cell

 


**Absolute threshold control
is hard**
**Unprogrammed transistor
might be depletion**
⇒ **2 transistor cell**

Flash EEPROM

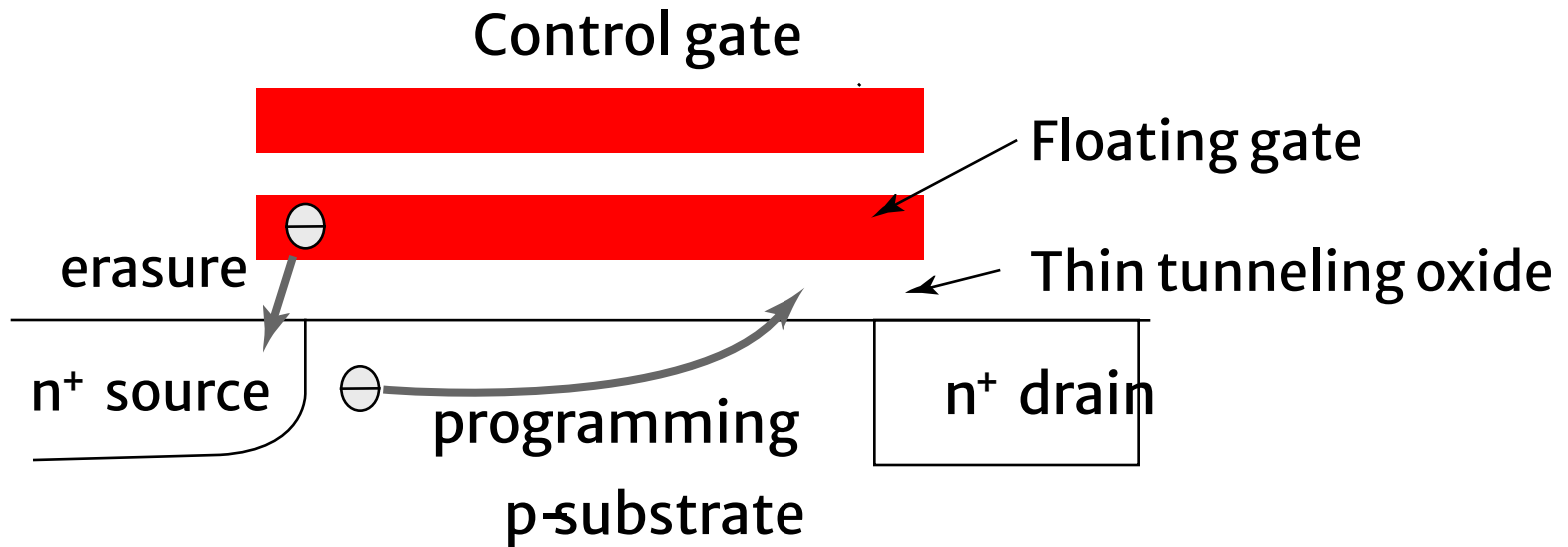

Many other options ...



Cross-sections of NVM cells

 



Flash

EPROM

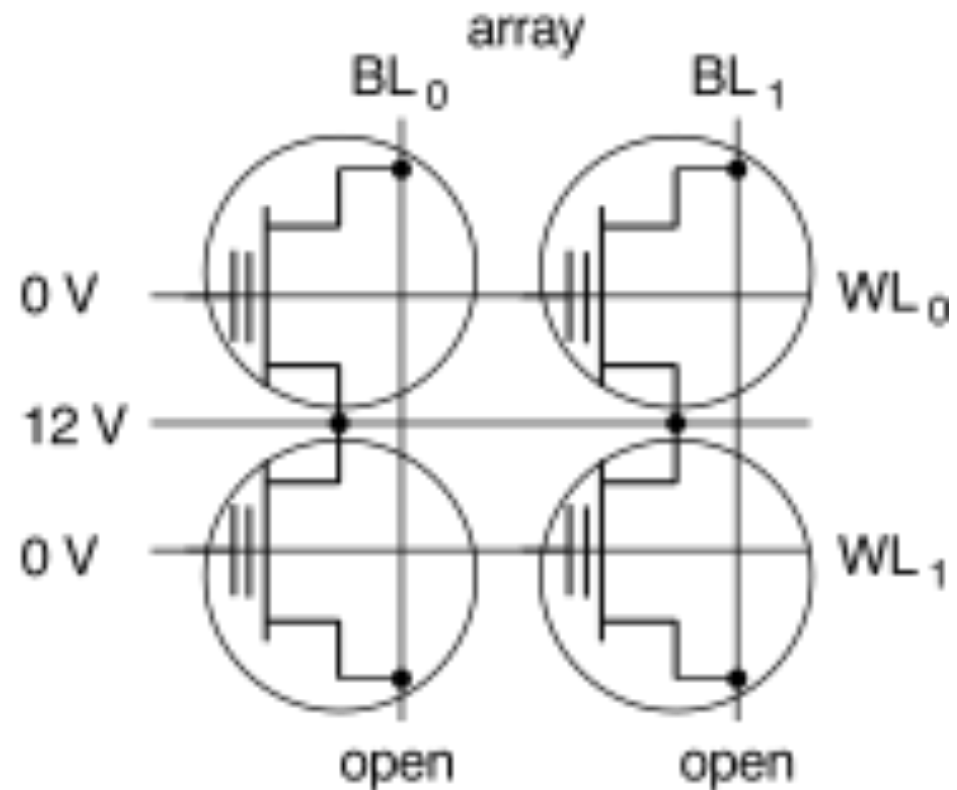
 
Basic Operations in a NOR Flash Memory—Erase



  Basic Operations in a NOR Flash Memory—Read



NAND Flash Memory

 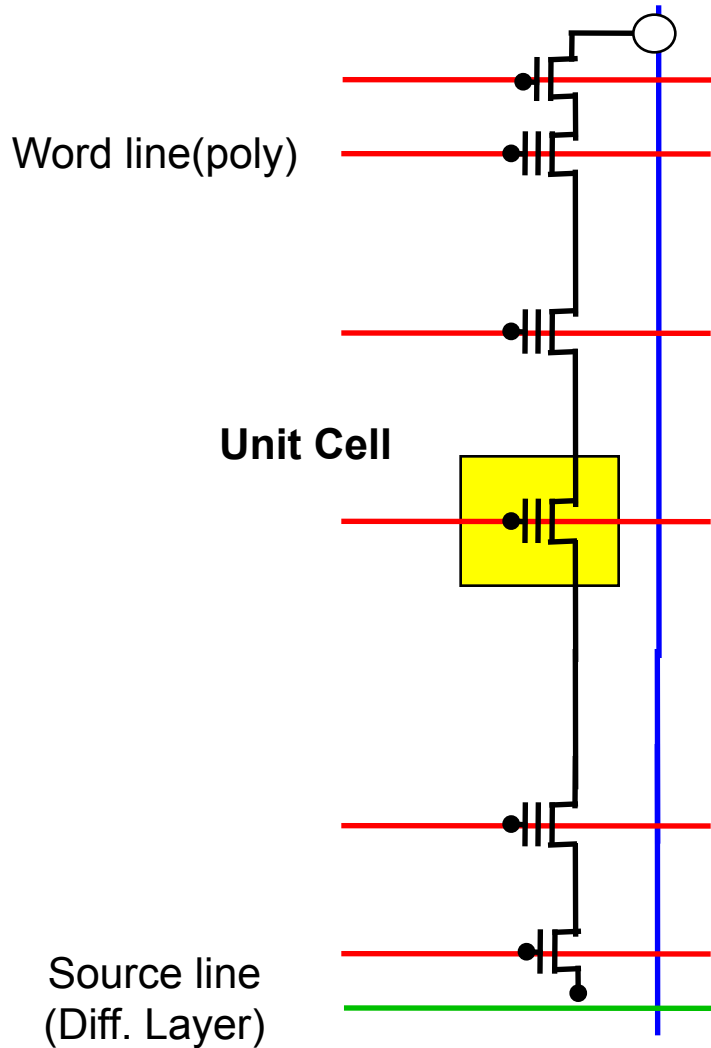


NAND Flash READ

- Pull $n-1$ bit lines above programmed V_{th} to turn them on
- One pulled above V_{th} of an erased bit
- Will pull down iff selected bit has NOT been programmed



NAND Flash WRITE/ERASE

- ERASE sets all bits to 1
 - Charges floating gates ($V_g=0V$, $V_s=12V$)
- WRITE can only set bits to 0
 - Discharges floating gates ($V_g=12V$, $V_d=6V$)
- Can WRITE as long as 0's are subset of 1's
 - Ex. Write 1111 then 1110 then 1010 etc.
- External RAM needed to cache results during ERASE/WRITE



Sky130 64x64 Flash Array + Sense Amps

 

NAND Flash and Sense Amp

  


Left: Programmed, Right: Cleared

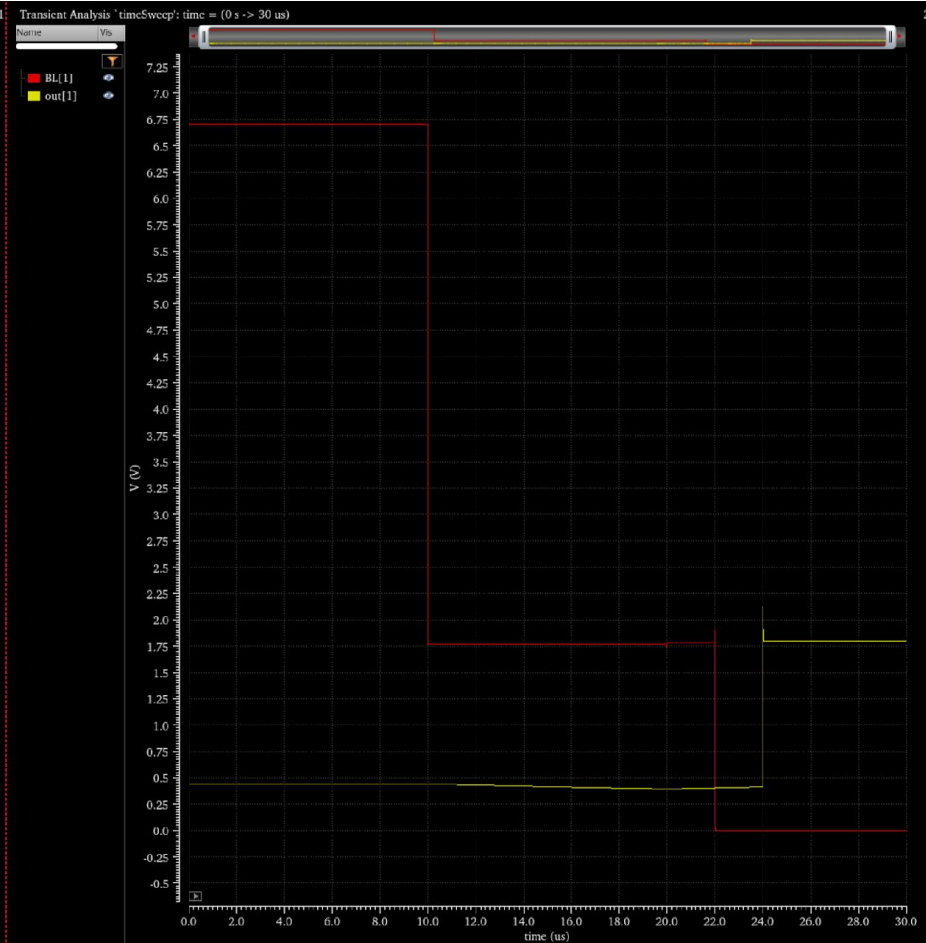 


Wear Leveling

- Each programming of floating gate damages the oxide
 - Limited number of writes (10k-100k?)
- Wear leveling can remap frequently written addresses to “even out” wear
- Requires programmable address decoding
- Increases write lifetime to 100k-1M

ReRAM

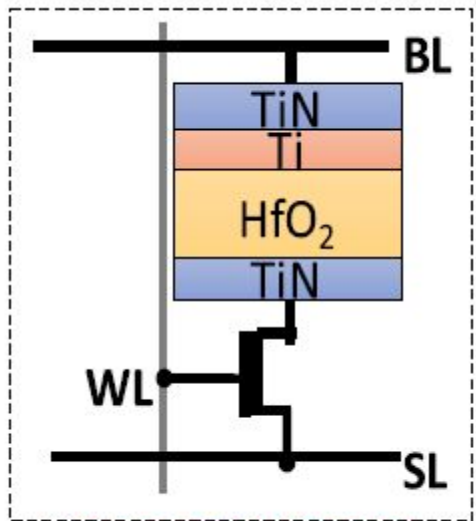


1T1R RRAM CELL

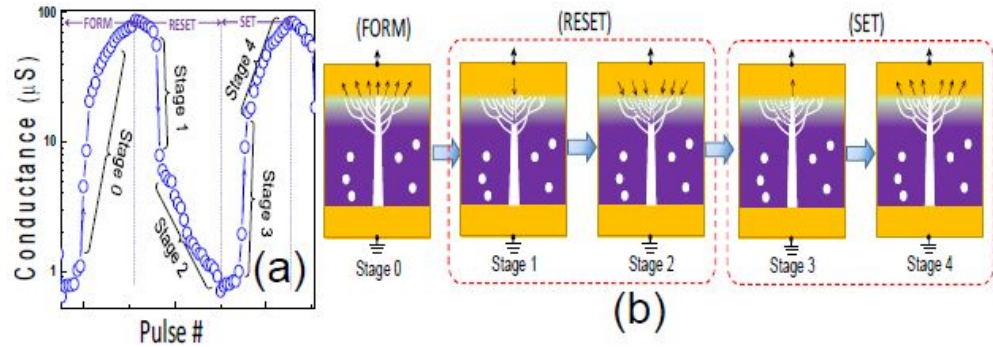



Hsieh et al, High-Density Multiple Bits-per-Cell 1T4R RRAM Array with Gradual SET/RESET and its Effectiveness for Deep Learning

Sneak Paths in Crossbar Arrays

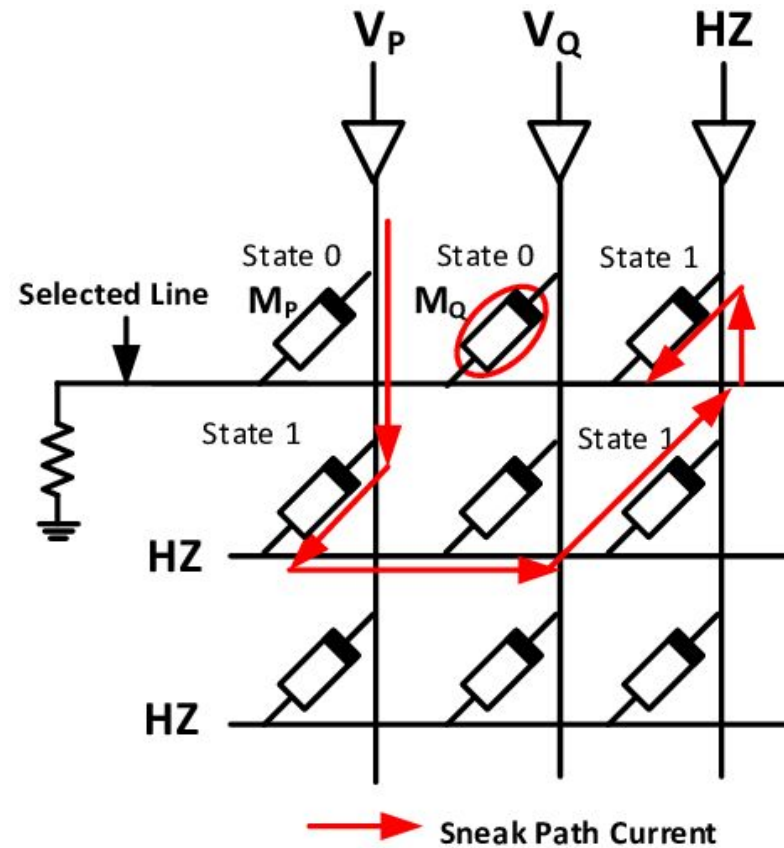

Form, Reset, and Set

1T1R #5	WL (V)	BL (V)	SL (V)	PW (ns)
Pristine				
Form	1.4 – 2.0 (0.1 step)	2.6 – 3.1 (0.1 step)	0	1000
Reset	2.5	0	2.6	1000
Set	1.7	2.4	0	1000

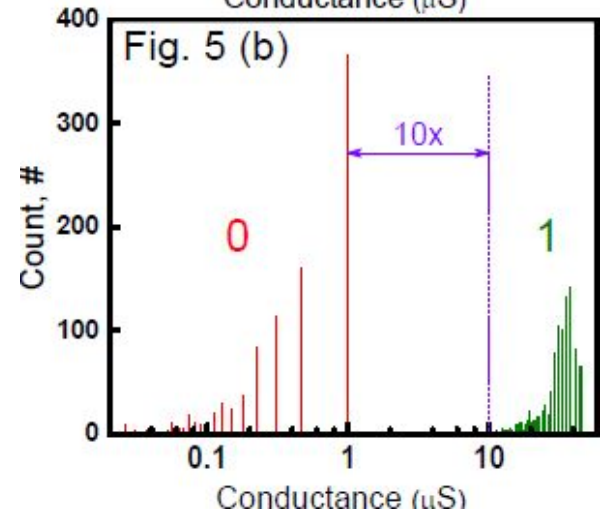 


Le et al, Resistive RAM With Multiple Bits Per Cell: Array-Level Demonstration of 3 Bits Per Cell, IEEE Electron Devices, 2019.






Lecture 15

Hsieh et al, High-Density Multiple Bits-per-Cell 1T4R RRAM Array with Gradual SET/RESET and its Effectiveness for Deep Learning

1T1R Multilevel

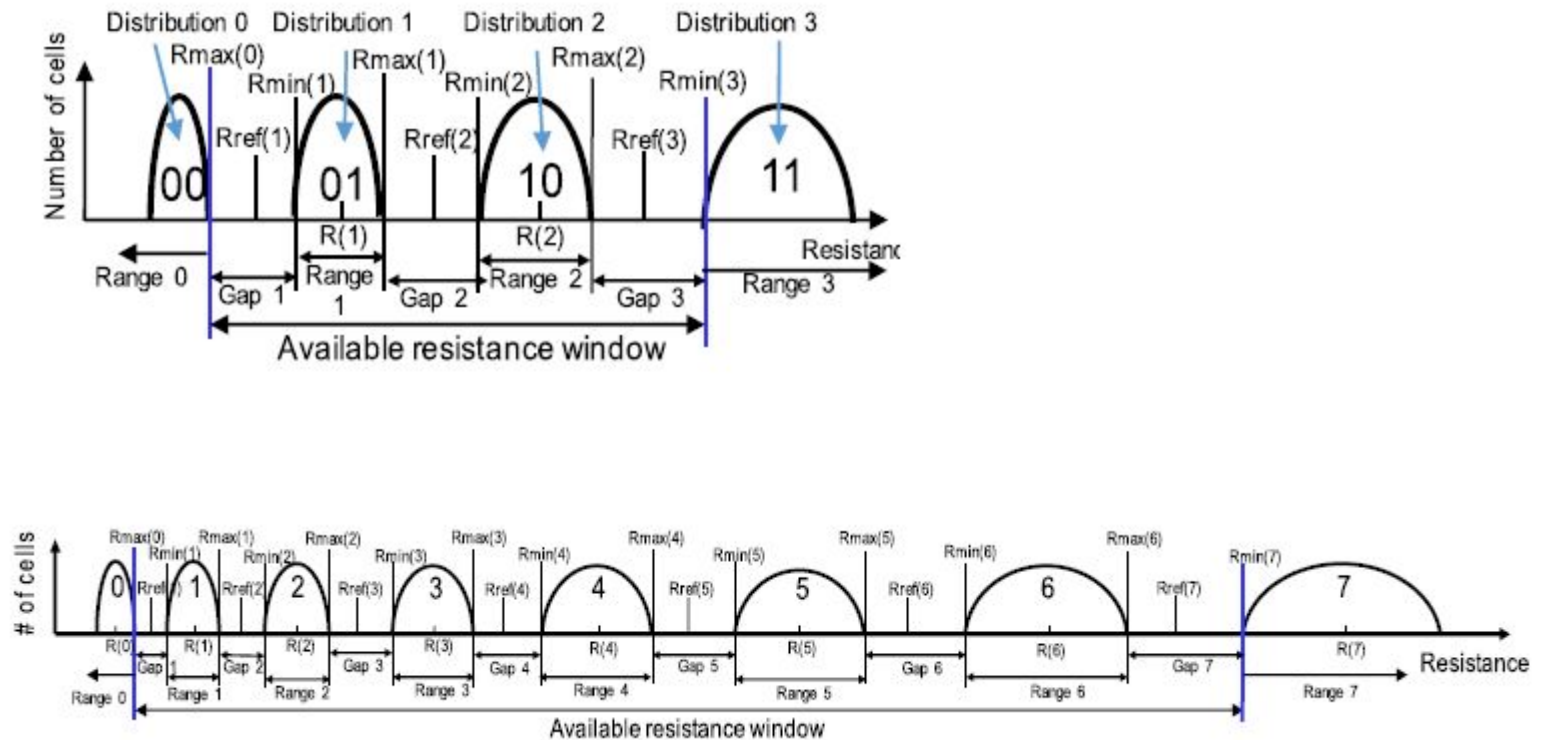

1T4R

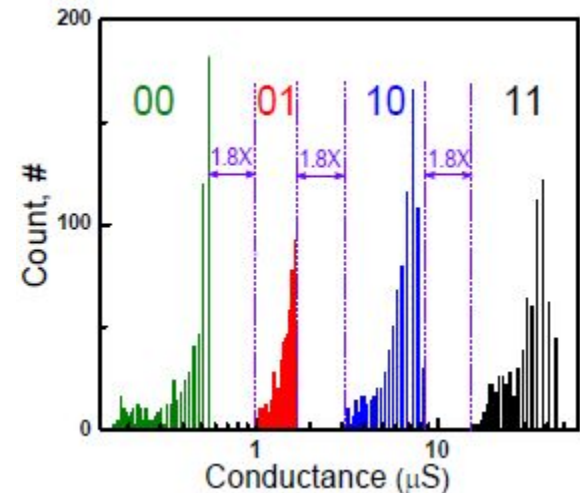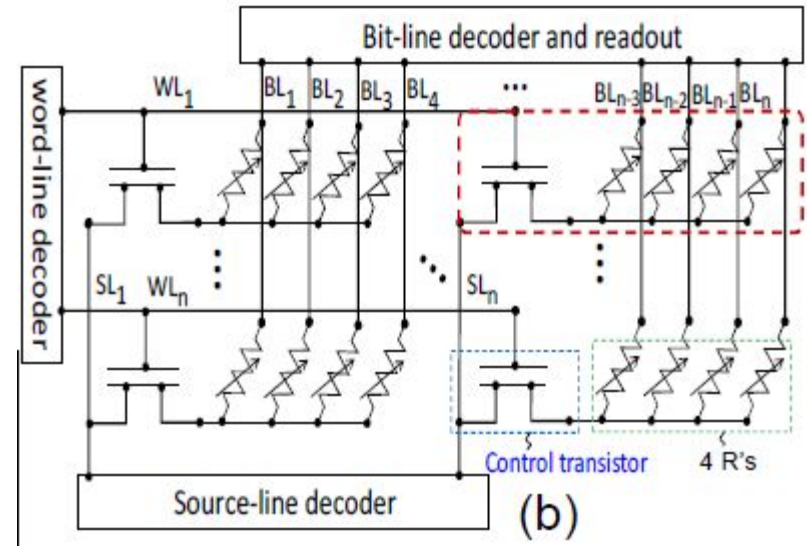   

Summary

- Memory performance is critical to overall system performance
- On-chip SRAM very common today
 - 6T SRAM cells have become very compact
 - Complete memory architecture involves arrays + row/column decoders, sense amps, output drivers
- Nonvolatile memory has grown just as important.